
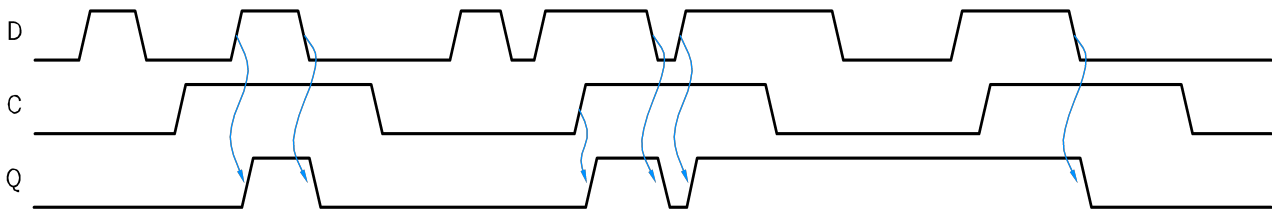


■ Quando $C=1$:

- $Q=D$

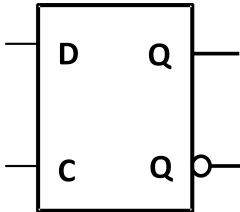

Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

